

LAB A5 Report

TT0L - GROUP 0

Person 1	111111111@student.mmu.edu.my
Person 2	111111111@student.mmu.edu.my

1. Design a 3 input priority encoder circuit. The inputs are $a_3a_2a_1$, with a_3 having the lowest priority and a_1 the highest. The outputs are y_2y_1 , indicating the encoded highest-priority active input, and v , the valid output which indicates that at least one input is active. (Note: Priority input a_3 is encoded as 11, a_2 as 10 and a_1 as 01)

Perform the following:

- I. Construct the truth table

a3	a2	a1	y2	y1	v
0	0	0	x	x	0
0	0	1	0	1	1
0	1	0	1	0	1
0	1	1	0	1	1
1	0	0	1	1	1
1	0	1	0	1	1
1	1	0	1	0	1
1	1	1	0	1	1

- II. Simplify the Boolean expressions for y_2 , y_1 , and v using Karnaugh map techniques.

a_3/a_2a_1	00	01	11	10
0	x	0	0	1
1	1	0	0	1

$$y_2 = \overline{a_1}$$


a_3/a_2a_1	00	01	11	10
0	x	1	1	0
1	1	1	1	0

$$y_1 = \overline{a_2} + a_1$$

a_3/a_2a_1	00	01	11	10
0	0	1	1	1
1	1	1	1	1

$$v = a_3 + a_2 + a_1$$

 - III. Draw the logic diagram with necessary basic logic gates.
 IV. Verify your design experimentally



2. Design and construct a 3 to 8 decoder circuit using 2-line-to-4-line decoder and also other logic gates needed.



Perform the following:

- I. Form the truth table for higher order decoder (3 to 8 decoder)


X	Y	Z	D0	D1	D2	D3	D4	D5	D6	D7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

A	B	D0	D1	D2	D3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1


E	A	B	D0	D1	D2	D3
0	X	X	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

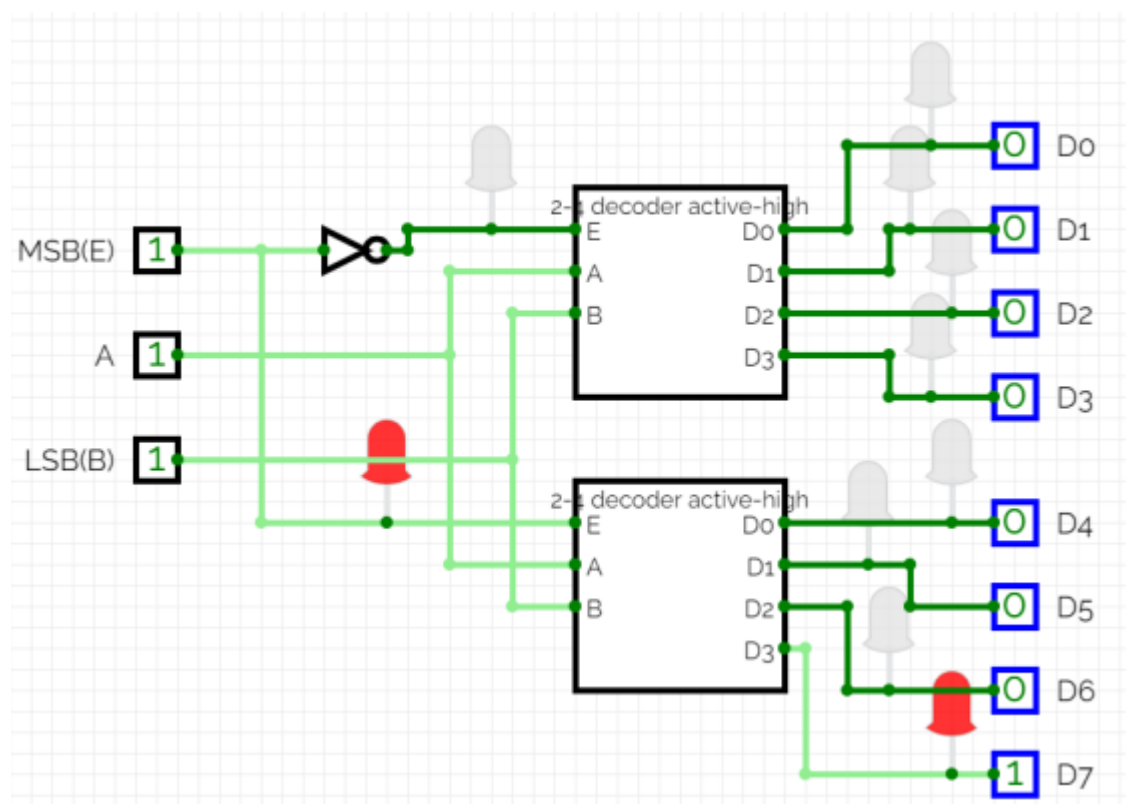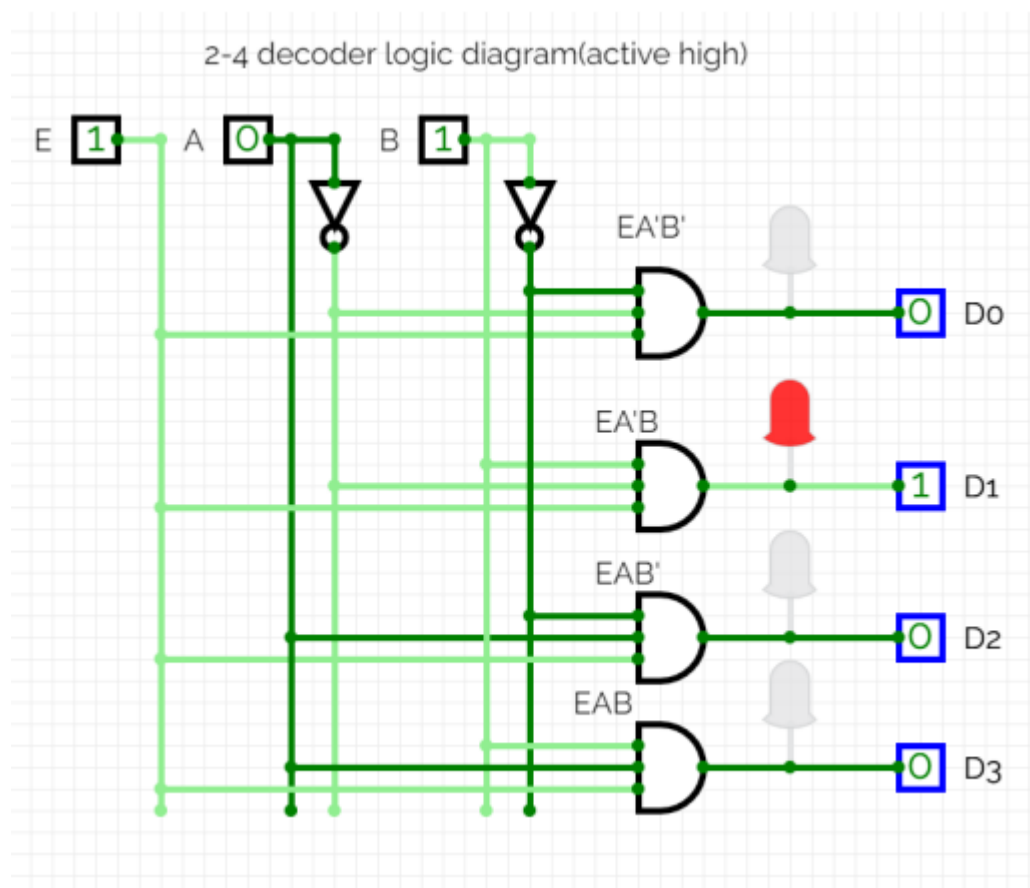

 
3. Design a full adder circuit using
 - I. Two half adders



II. Using only NAND gates

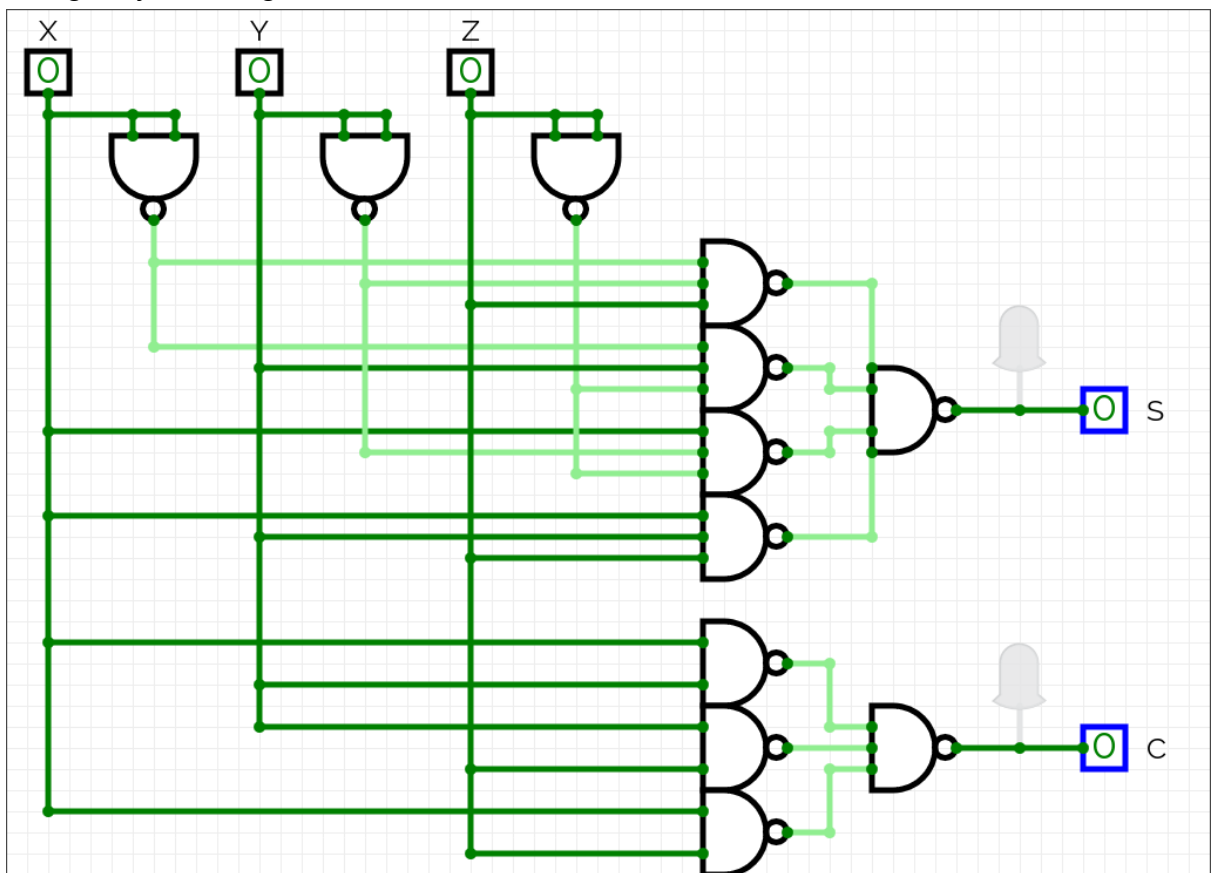

III. Using Only NOR gates

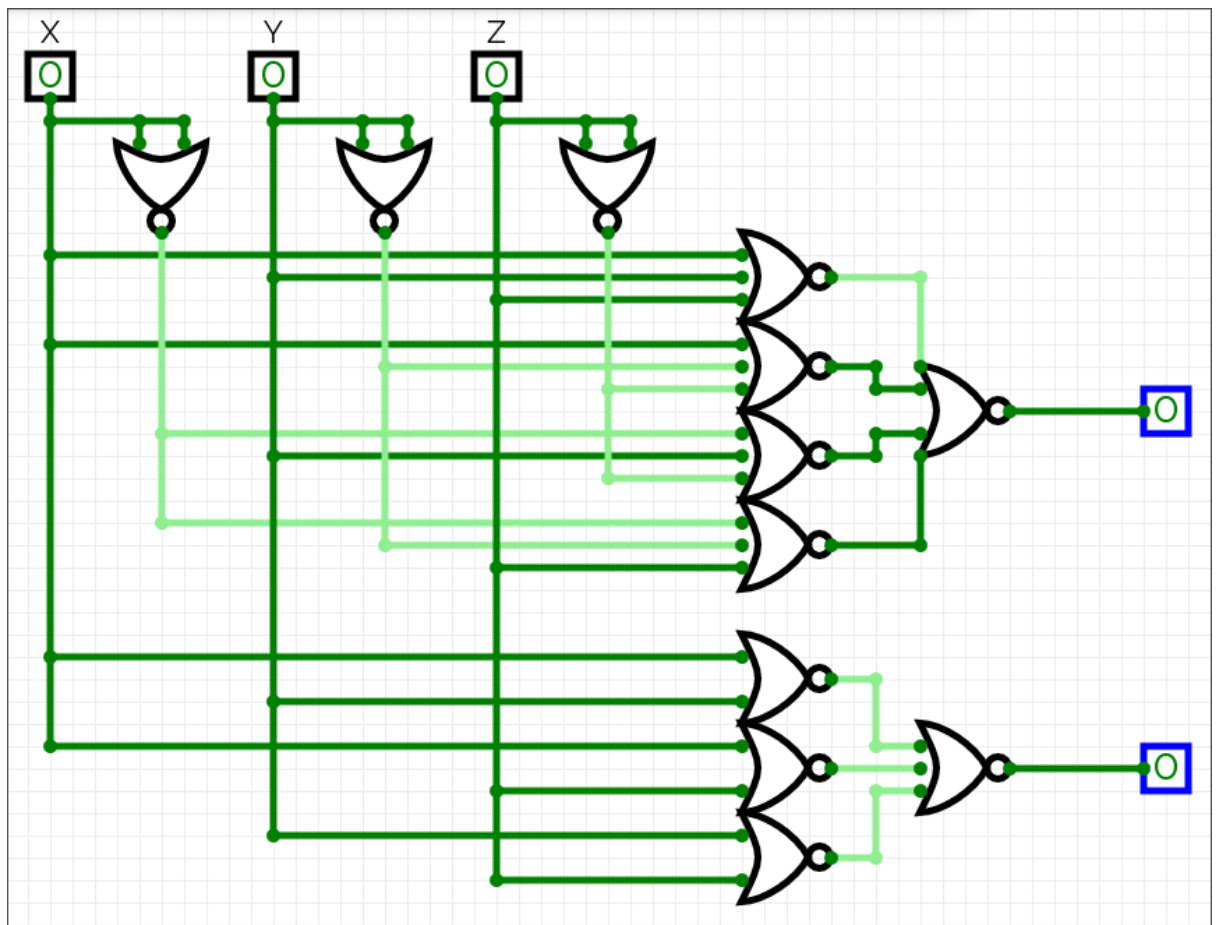


4. Implement the following Boolean expression


$$F(W, X, Y, Z) = \Sigma m(1, 2, 4, 6, 7, 9, 11, 14, 15)$$

W	X	Y	Z	F
0	0	0	0	0
0	0	0	1	1 F=Z
0	0	1	0	1
0	0	1	1	0 F=Z'
0	1	0	0	1
0	1	0	1	0 F=Z'
0	1	1	0	1
0	1	1	1	1 F=1
1	0	0	0	0
1	0	0	1	1 F=Z
1	0	1	0	0
1	0	1	1	1 F=Z
1	1	0	0	0
1	1	0	1	0 F=0
1	1	1	0	1
1	1	1	1	1 F=1

 
I. Using 8×1 MUX and the needed logic gates



 II. Using 16 ×1 MUX and the needed logic gates



 III. Using a suitable decoder and an OR gate



5. Design code converter circuits for the following problems.

I. 3-bit Gray-to- binary code converter

Gray Code	Binary
000	000
001	001
011	010
010	011
110	100
111	101
101	110
100	111

g_2/g_1g_0	00	01	11	10
0	0	0	0	0
1	1	1	1	1


$$b_2 = g_2$$

g_2/g_1g_0	00	01	11	10
0	0	0	1	1
1	1	1	1	1

$$b_1 = g_1 \oplus b_2$$

$g_2/g_1/g_0$	00	01	11	10
0	0	1	0	1
1	1	0	1	0

$$b_0 = g_0 \oplus b_1$$

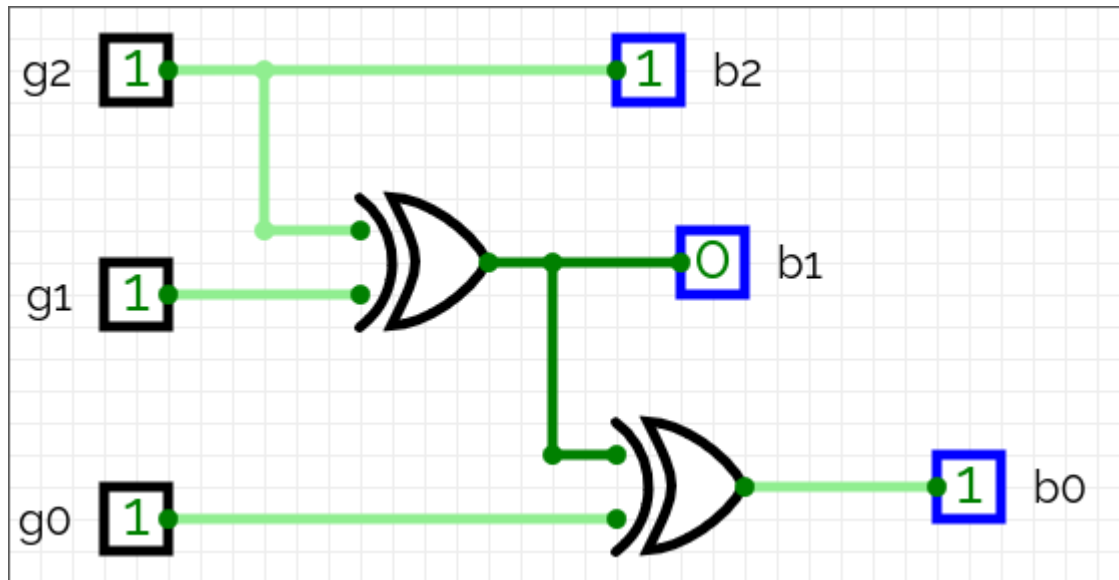

II. 3-bit Binary-to-Gray code converter

Binary b2b1b0	Gray Code g2g1g0
000	000
001	001
010	011
011	010
100	110
101	111

110	101
111	100

b2/b0b1	00	01	11	10
0	0	0	0	0
1	1	1	1	1


$$g2 = b2$$

b2/b0b1	00	01	11	10
0	0	0	1	1
1	1	1	0	0

$$g1 = b1 \oplus g2$$

$$g0 = b0 \oplus b1$$

b2/b0b1	00	01	11	10
0	0	1	0	1
1	0	1	0	1

 

III. (8 4 -2 -1) BCD code to (Excess 3) BCD code converter

INPUTS				OUTPUTS			
A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	1	1
0	1	1	1	0	1	0	0
0	1	1	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	0	0	0	1	1	1
1	0	1	1	1	0	0	0
1	0	1	0	1	0	0	1
1	0	0	1	1	0	1	0
1	0	0	0	1	0	1	1
1	1	1	1	1	1	0	0

AB/CD	00	01	11	10
00	0	X	X	X
01	0	0	0	0
11	X	X	1	X
10	1	1	1	1

$$W = A$$

AB/CD	00	01	11	10
00	0	X	X	X
01	1	1	1	1
11	X	X	1	X
10	0	0	0	0

$$X = B$$

AB/CD	00	01	11	10
00	1	X	X	X
01	1	1	0	0
11	X	X	0	X
10	1	1	0	0

$$Y = C'$$

AB/CD	00	01	11	10
00	1	X	X	X
01	1	0	0	1
11	X	X	0	X

10	1	0	0	1
----	---	---	---	---

$$Z = D'$$

